
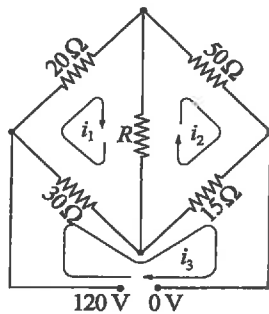


12. ■ The displacement formulation for the mass-spring system shown in Fig. (a) results in the following equilibrium equations of the masses

$$\begin{bmatrix} k_1 + k_2 + k_3 + k_5 & -k_3 & -k_5 \\ -k_3 & k_3 + k_4 & -k_4 \\ -k_5 & -k_4 & k_4 + k_5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} W_1 \\ W_2 \\ W_3 \end{bmatrix}$$

where  $k_i$  are the spring stiffnesses,  $W_i$  represent the weights of the masses, and  $x_i$  are the displacements of the masses from the undeformed configuration of the system. Write a program that solves these equations for given  $k$  and  $W$ . Use the program to find the displacements if

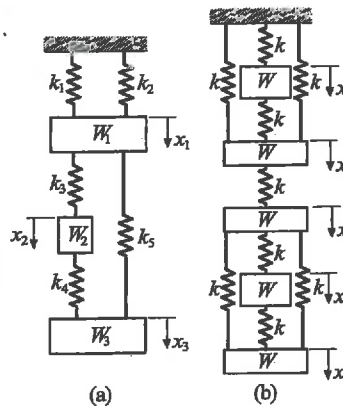
$$\begin{aligned} k_1 = k_3 = k_4 = k & & k_2 = k_5 = 2k \\ W_1 = W_3 = 2W & & W_2 = W \end{aligned}$$



The electrical network shown can be viewed as consisting of three loops. Applying Kirchoff's law ( $\sum \text{voltage drops} = \sum \text{voltage sources}$ ) to each loop yields the following equations for the loop currents  $i_1$ ,  $i_2$  and  $i_3$ :

$$\begin{aligned} (50 + R)i_1 - Ri_2 - 30i_3 &= 0 \\ -Ri_1 + (65 + R)i_2 - 15i_3 &= 0 \\ -30i_2 - 15i_2 + 45i_3 &= 120 \end{aligned}$$

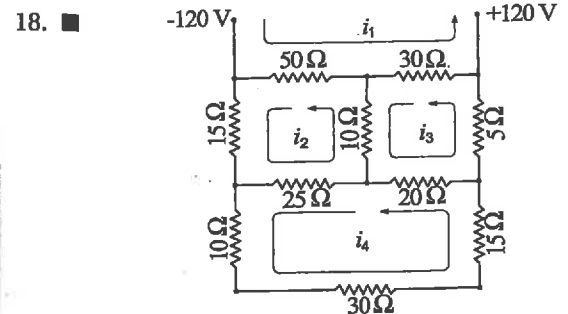Compute the three loop currents for  $R = 5 \Omega$ ,  $10 \Omega$ , and  $20 \Omega$ .



Determine the loop currents  $i_1$  to  $i_4$  in the electrical network shown.